## SCHOOL OF COMPUTER ENGINEERING

## 1 Sem M.Tech. (Computer Science and Engineering)

## Mid Semester Exam

**SUBJECT: CSS 5104 Quantum Computing** 

Time: 2.15 PM-3.45 PM

Date: 16-09-2025

MAX.MARKS: 30

**Note: Answer All Questions** 

1A. Define "braket" of two vectors  $|v\rangle$  and  $|w\rangle$ . If

$$|v\rangle = \frac{2i}{\sqrt{5}}|0\rangle + \frac{1}{\sqrt{5}}|1\rangle$$
 and  $|w\rangle = \frac{2}{\sqrt{5}}|0\rangle - \frac{i}{\sqrt{5}}|1\rangle$ , compute  $\langle v|w\rangle$ . (3M)

1B. Let 
$$|v\rangle = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$
 and  $|w\rangle = \begin{bmatrix} w_1 \\ w_2 \end{bmatrix}$  compute  $v \otimes w$ . Let  $|\psi\rangle = \frac{1}{\sqrt{2}} (|00\rangle + |11\rangle)$ , compute P(00)

and P(11). Let H and I are Hadamard and Identity gates respectively, evaluate  $|\psi_1\rangle = (H \otimes I)|\psi\rangle$ . (5M)

1C. With neat diagram, explain Bloch sphere. (2M)

2A. Imagine we can define a unitary operator U that can copy the qubit states  $|0\rangle and |1\rangle : U(|0\rangle|0\rangle) = |0\rangle|0\rangle and U(|1\rangle|0\rangle) = |1\rangle|1\rangle$ . Can U be used to copy  $|\psi\rangle = \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle)$  Verify using an explicit calculation. (4M)

2B. Define Z gate and give its bracket representation. (3M)

2C. State No-Cloning Theorem. With quantum circuit, show that the unknown quantum state  $|\psi\rangle = a|0\rangle + b|1\rangle$  cannot be copied using CNOT gate. (3M)

3A. Define Bell state. Consider the following quantum circuit:



Compute the outputs for the inputs:  $|00\rangle, |01\rangle, |10\rangle$  and  $|11\rangle$ . (5M)

3B. With circuit diagram, implement SWAP operation using CNOT gate. (2M)

3C. Define CCNOT gate. Design its quantum circuit and matrix representation. With quantum circuit implement OR gate using CCNOT gate. (3M)